 


# Exercise 13 (UART Transmitter)(HW3 Prob4):

- RS-232 signal phases
  - Idle
  - Start bit
  - Data (8-data for our project)
  - Parity (no parity for our project)
  - Stop bit – channel returns to idle condition
  - Idle or Start next frame




Baud rate will be 9600 with 50MHz clock → 5208 divider → 13-bit



- Transmitter sits idle till told to transmit. Then will shift out a 9-bit (start bit appended) register at the baud rate interval.


## Exercise 13 (UART Transmitter)

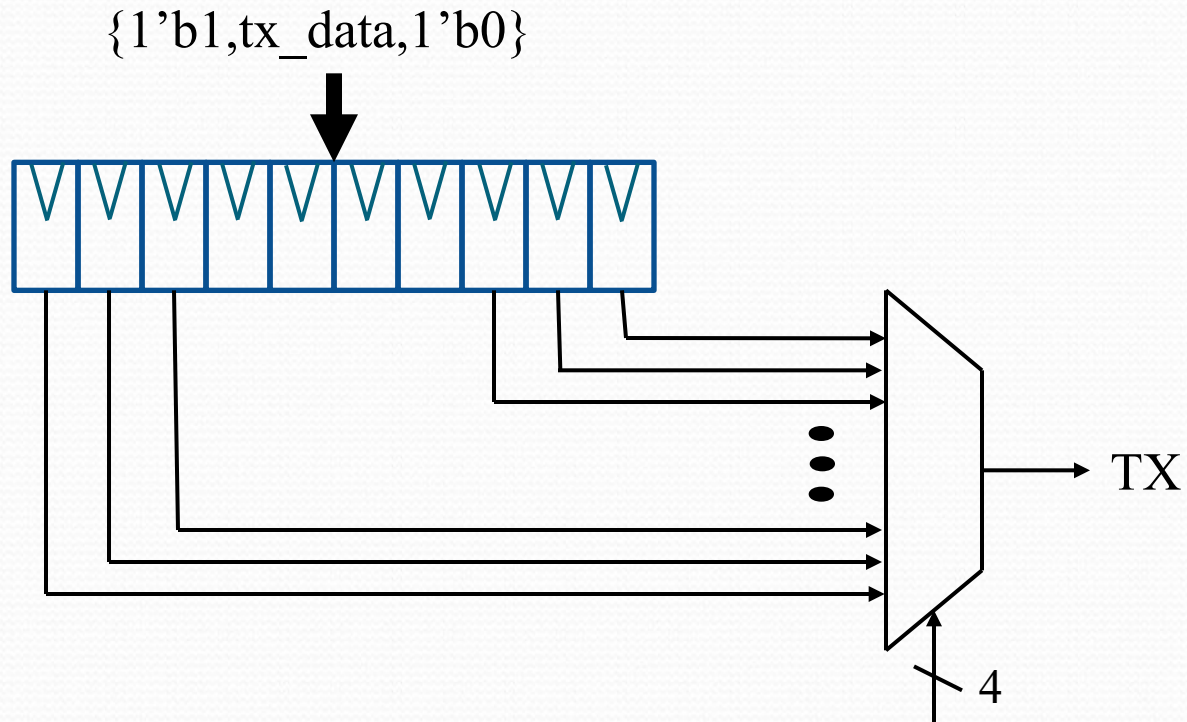




## Exercise 13 (UART Transmitter)

$\{1'b1, tx\_data, 1'b0\}$

 


A simple shift reg is heart of the machine

$\{tx\_data, 1'b0\}$

 

Does not even have to be 10-bits, can get away with 9.

# Possible Topology of UART\_tx

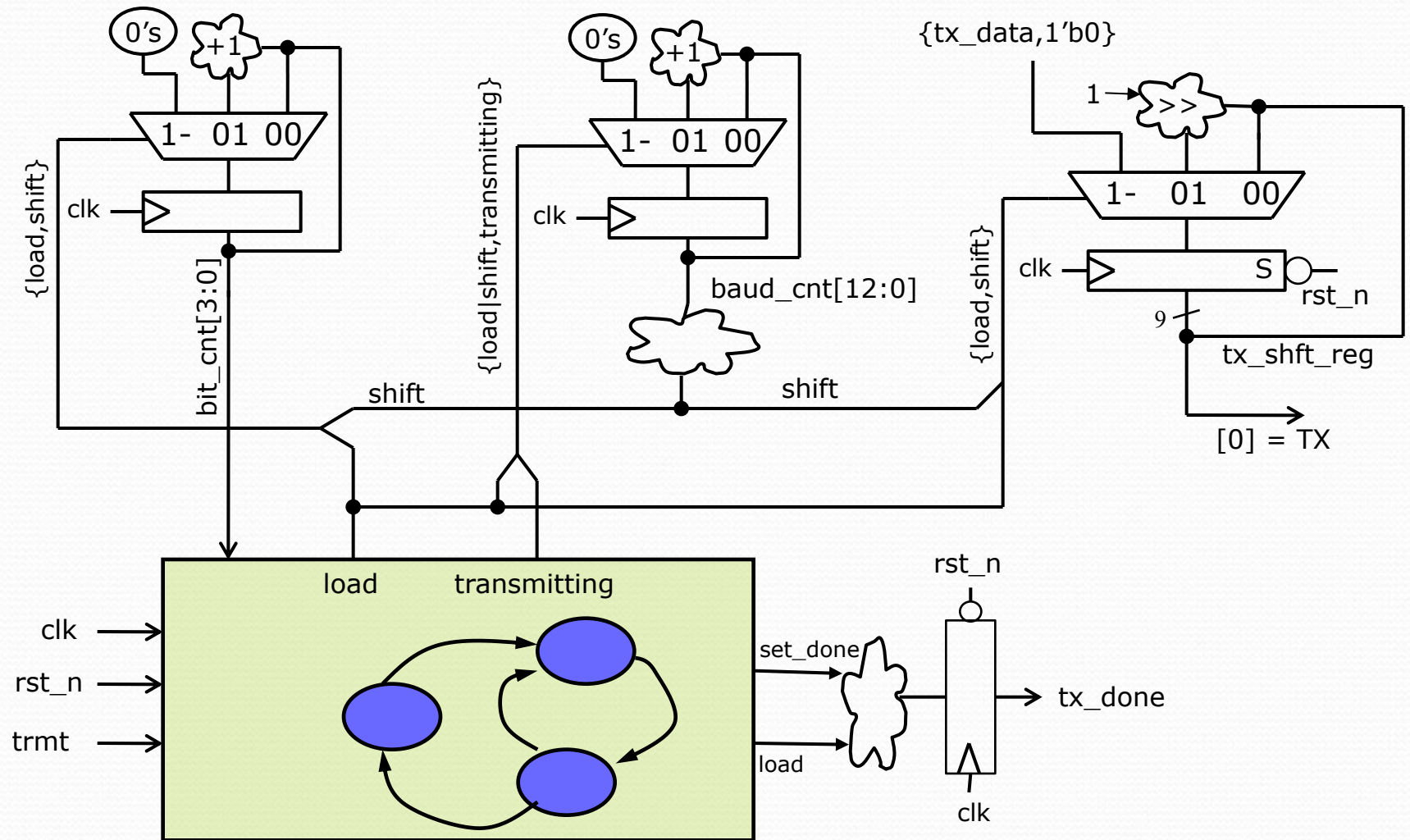




# Warning on use of LLM

- Copilot/LLM usage will likely result in a functional UART transmitter. This is the kind of well defined functional block that it does well.
- However, keep in mind your objective is not to get it done, or even necessarily to learn. Your objective is to produce code in a style that Eric likes, and that will synthesize efficiently. So....guide your LLM to produce that.

## Exercise 13 (UART Transmitter):

 

Signal:	Dir:	Description
clk,rst_n	in	50MHz system clock & active low reset
TX	out	Serial data output
trmt	in	Asserted for 1 clock to initiate transmission
tx_data[7:0]	in	Byte to transmit
tx_done	out	Asserted when byte is done transmitting. Stays high till next byte transmitted.

- HW3 Problem 4 involves making a UART transmitter (*UART\_tx.sv*). You are to start that design during this exercise.
- Make a simple test bench for it. Just instantiate your transmitter and send a few bytes. Verify correct functionality (including baud rate) by looking at the waveforms.
- Submit *UART\_tx.sv* to the dropbox for Exercise13.