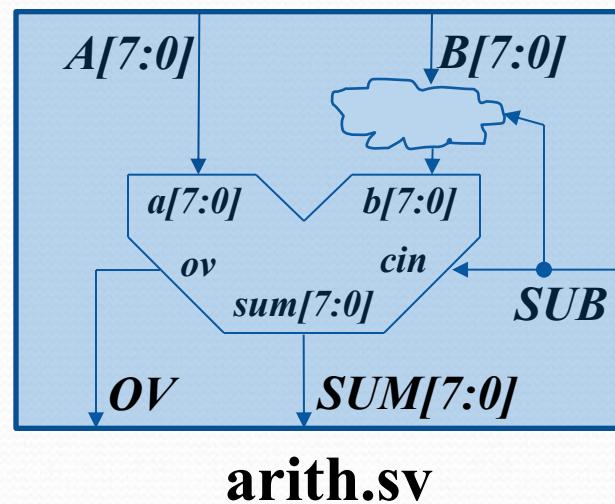


# Exercise 5 (Testbench for Arithmetic Block):


- You will create a testbench for an 8-bit arithmetic block.
  - Arithmetic unit can perform addition or subtraction.

$$\begin{aligned} \text{SUM} &= A + B \text{ if } \text{SUB is low} \\ \text{SUM} &= A - B \text{ if } \text{SUB is high} \end{aligned}$$

- Arithmetic unit also outputs an overflow signal if the result is either too positive or too negative to represent as an 8-bit **signed** number.
- Code for DUT (**arith.sv**) is provided.



# Test Benches with Verilog

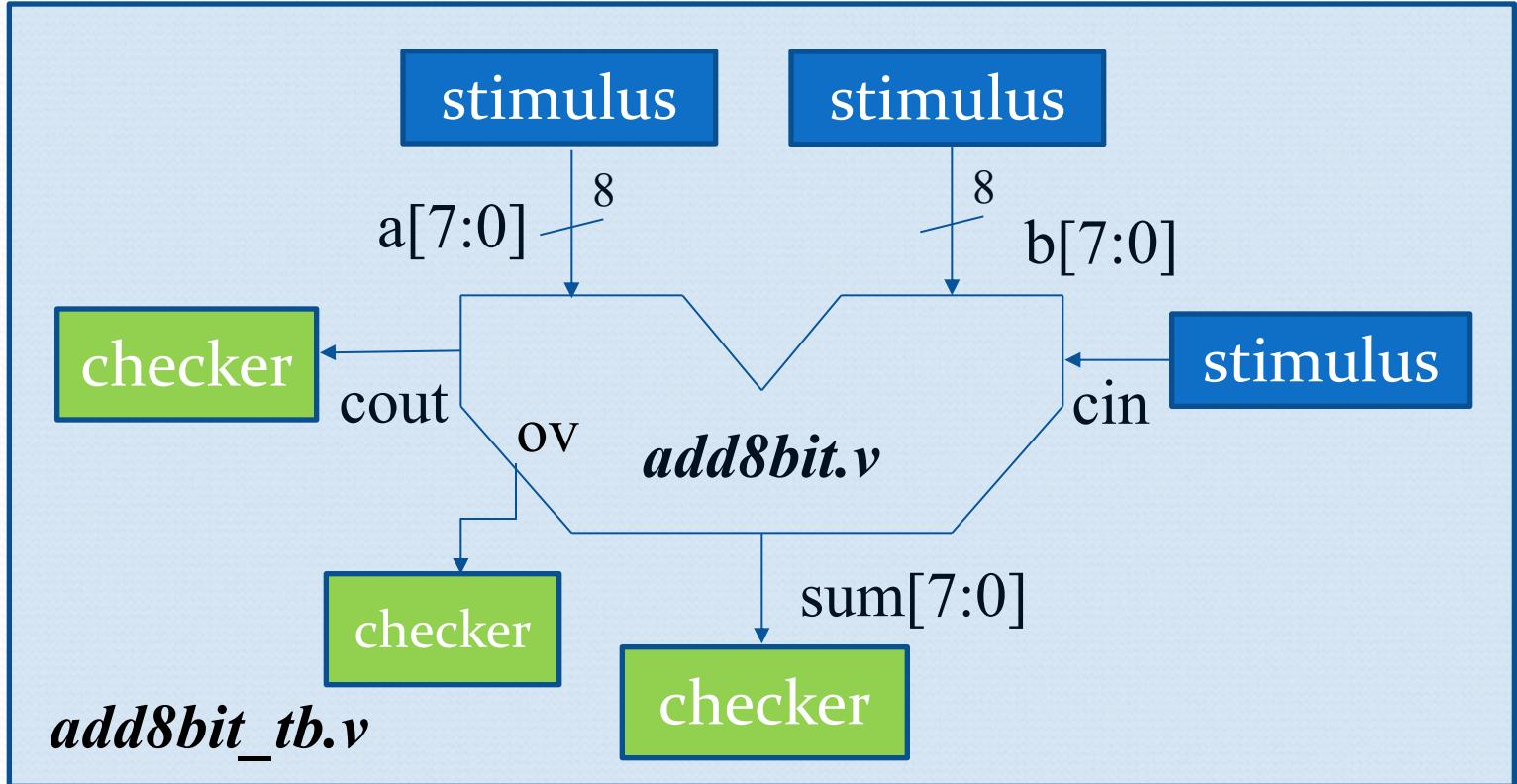

- Elements of a test bench.
  - Instantiate DUT
  - Apply Stimulus
  - Good test bench also checks results

# Test Bench Example:

I use type **reg** for stimulus and type **wire** for monitoring outputs because I am an old man who can't change his ways. You use type **logic** for both.

```
module add8bit_tb();  
  
reg [7:0] stm_a,stm_b; // used as stimulus for a,b  
reg stm_cin; // used as stimulus for cin  
  
wire [7:0] sum_mon; // used to monitor sum  
wire cout_mon,ov_mon; // used to monitor cout & ov  
  
add8bit iDUT(.a(stm_a), .b(stm_b), .cin(stm_cin),  
             .cout(cout_mon), .sum(sum_mon),  
             .ov(ov_mon));  
  
initial begin  
    stm_a = 8'hA5;  
    stm_b = 8'h5A;  
    stm_cin = 0; // result should be FF  
    #5; // wait 5 time units  
    ... // I expect more stimulus  
end  
  
endmodule
```

## Exercise 5 (Testbench for Arithmetic Block):

- Your testbench is for **arith.sv** (*what I showed was for an adder only block*)
  - The stimulus you apply should test both addition and subtraction
  - The stimulus you apply should test for overflow conditions.
  - **arith.sv** contains a bug in the **ov** logic. See if your testbench can find it.
  - Your testbench should include commenting telling what you are trying to test. It does not have to be self checking. We will work on that more in the future.
  - You can use AI/LLM for generating the template of the testbench, but it is best if you think of the corner conditions to test on your own.
  - Submit **arith\_tb.sv**, and waveforms showing you ran it to the dropbox
  - Submit a fixed version of **arith.sv** (*fixing the bug in the **ov** logic*)